

I had a **bright idea** at SMUD





Electric circuit maker project brought to you by the
Energy Education & Technology Center.

To register for workshops, request hardcopies of this template,
download copies, or find out where to purchase materials visit
smud.org/Education.

Powering forward.
Together.



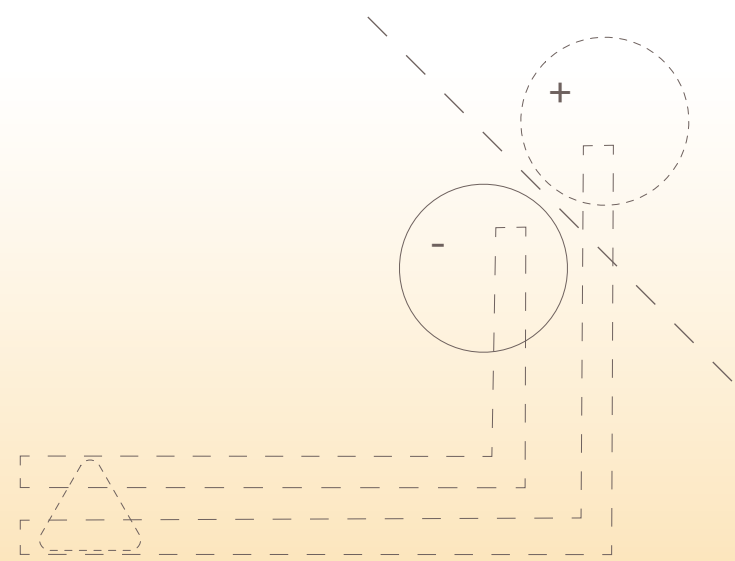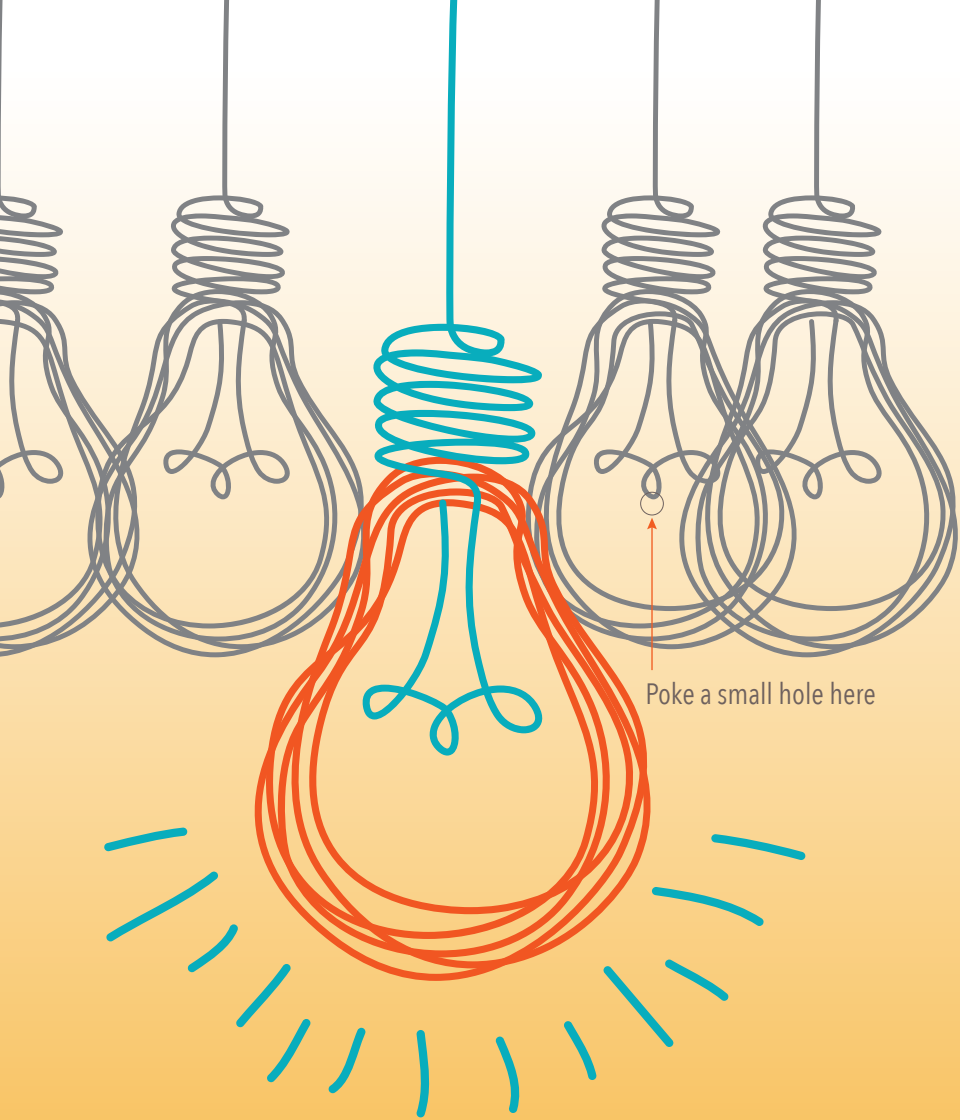

To turn on the light:

1. Place **copper adhesive tape** on template, bending 90° at the corners.
2. Place **LED sticker** on template.
3. Poke a **hole** with a pin to allow LED light to shine through the cover.
4. Place **button battery** on the solid circle, positive side up. You may use double sided tape or glue (avoid the copper tape).
5. Fold along **dotted line** to complete the circuit and light up LED.
6. Close cover and see LED light shine.

To electrify your world with more maker projects visit smud.org/Education.